

# RAJALAKSHMI ENGINEERING COLLEGE

## DEPARTMENT OF ECE

### ANALOG CIRCUITS I

#### UNIT I

#### DESIGN FORMULAS

##### Equations

$$r_e = \frac{26 \text{ mV}}{I_E}$$

Hybrid parameters:

$$h_{ie} = \beta r_e, \quad h_{fe} = \beta_{ac}, \quad h_{ib} = r_e, \quad h_{fb} = -\alpha \cong -1$$

CE fixed bias:

$$Z_i \cong \beta r_e, \quad Z_o \cong R_C$$

$$A_v = -\frac{R_C}{r_e}, \quad A_i = -A_v \frac{Z_i}{R_C} \cong \beta$$

Voltage-divider bias:

$$Z_i = R_1 \parallel R_2 \parallel \beta r_e, \quad Z_o \cong R_C$$

$$A_v = -\frac{R_C}{r_e}, \quad A_i = -A_v \frac{Z_i}{R_C} \cong \beta$$

CE emitter-bias:

$$Z_i \cong R_B \parallel \beta R_E, \quad Z_o \cong R_C$$

$$A_v \cong -\frac{R_C}{R_E}, \quad A_i \cong \frac{\beta R_B}{R_B + \beta R_E}$$

Emitter-follower:

$$Z_i \cong R_B \parallel \beta R_E, \quad Z_o \cong r_e$$

$$A_v \cong 1, \quad A_i = -A_v \frac{Z_i}{R_E}$$

Common-base:

$$Z_i \cong R_E \parallel r_e, \quad Z_o \cong R_C$$

$$A_v \cong \frac{R_C}{r_e}, \quad A_i \cong -1$$

Collector feedback:

$$Z_i \cong \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}, \quad Z_o \cong R_C \parallel R_F$$

$$A_v = -\frac{R_C}{r_e}, \quad A_i \cong \frac{R_F}{R_C}$$

Collector dc feedback:

$$Z_i \cong R_{F1} \parallel \beta r_e, \quad Z_o \cong R_C \parallel R_{F2}$$
$$A_v = -\frac{R_{F2} \parallel R_C}{r_e}, \quad A_i = -A_v \frac{Z_i}{R_C}$$

Cascode connection:

$$A_v = A_{v1} A_{v2}$$

Darlington connection (with  $R_E$ ):

$$\beta_D = \beta_1 \beta_2,$$

$$Z_i = R_B \parallel (\beta_1 \beta_2 R_E), \quad A_i = \frac{\beta_1 \beta_2 R_B}{(R_B + \beta_1 \beta_2 R_E)}$$

$$Z_o = \frac{r_{e1}}{\beta_2} + r_{e2} \quad A_v = \frac{V_o}{V_i} \approx 1$$

Darlington connection (without  $R_E$ ):

$$Z_i = R_1 \parallel R_2 \parallel \beta_1(r_{e1} + \beta_1 \beta_2 r_{e2}) \quad A_i = \frac{\beta_1 \beta_2 (R_1 \parallel R_2)}{R_1 \parallel R_2 + Z_i'}$$

where  $Z_i' = \beta_1(r_{e1} + \beta_2 r_{e2})$

$$Z_o \cong R_C \parallel r_{o2} \quad A_v = \frac{V_o}{V_i} = \frac{\beta_1 \beta_2 R_C}{Z_i'}$$

Feedback pair:


$$Z_i = R_B \parallel \beta_1 \beta_2 R_C \quad A_i = \frac{-\beta_1 \beta_2 R_B}{R_B + \beta_1 \beta_2 R_C}$$

$$Z_o \approx \frac{r_{e1}}{\beta_2} \quad A_v \cong 1$$

## SOLVED DESIGN PROBLEMS IN UNIT I

1. Design a audio amplifier using common emitter configuration and determine the following :

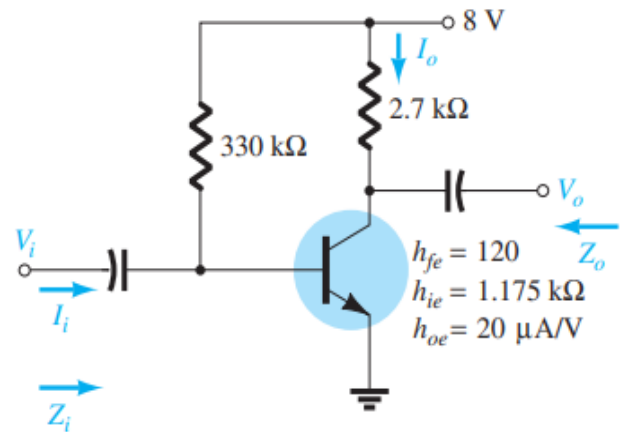- a.  $Z_i$ .
- b.  $Z_o$ .
- c.  $A_v$ .
- d.  $A_i$ .



**Solution:**

$$\text{a. } Z_i = R_B \parallel h_{ie} = 330 \text{ k}\Omega \parallel 1.175 \text{ k}\Omega \\ \cong h_{ie} = \mathbf{1.171 \text{ k}\Omega}$$

$$\text{b. } r_o = \frac{1}{h_{oe}} = \frac{1}{20 \mu\text{A/V}} = 50 \text{ k}\Omega$$


$$Z_o = \frac{1}{h_{oe}} \parallel R_C = 50 \text{ k}\Omega \parallel 2.7 \text{ k}\Omega = \mathbf{2.56 \text{ k}\Omega} \cong R_C$$

$$\text{c. } A_v = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}} = -\frac{(120)(2.7 \text{ k}\Omega \parallel 50 \text{ k}\Omega)}{1.171 \text{ k}\Omega} = \mathbf{-262.34}$$

$$\text{d. } A_i \cong h_{fe} = \mathbf{120}$$

2. Design a audio amplifier using common gate configuration and determine the following :

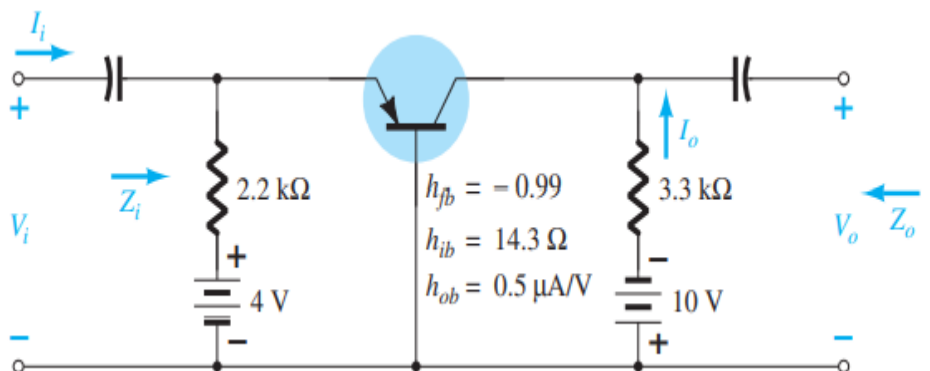- a.  $Z_i$ .
- b.  $Z_o$ .
- c.  $A_v$ .
- d.  $A_i$ .



**Solution:**

$$\text{a. } Z_i = R_E \parallel h_{ib} = 2.2 \text{ k}\Omega \parallel 14.3 \Omega = 14.21 \Omega \cong h_{ib}$$

$$\text{b. } r_o = \frac{1}{h_{ob}} = \frac{1}{0.5 \mu\text{A/V}} = 2 \text{ M}\Omega$$

$$Z_o = \frac{1}{h_{ob}} \parallel R_C \cong R_C = 3.3 \text{ k}\Omega$$

$$\text{c. } A_v = -\frac{h_{fb} R_C}{h_{ib}} = -\frac{(-0.99)(3.3 \text{ k}\Omega)}{14.21} = 229.91$$

$$\text{d. } A_i \cong h_{fb} = -1$$

**UNIT II****DESIGN FORMULAS****Equations**

JFET:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} |_{V_{GS}=0 \text{ V}}, \quad I_D = 0 \text{ mA} |_{V_{GS}=V_P}, \quad I_D = \frac{I_{DSS}}{4} |_{V_{GS}=V_P/2}, \quad V_{GS} \cong 0.3V_P |_{I_D=I_{DSS}/2}$$

$$V_{GS} = V_P \left( 1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

$$P_D = V_{DS} I_D$$

$$r_d = \frac{r_o}{(1 - V_{GS}/V_P)^2}$$

MOSFET (enhancement):


$$I_D = k(V_{GS} - V_T)^2$$

$$k = \frac{I_{D(\text{on})}}{(V_{GS(\text{on})} - V_T)^2}$$

**SOLVED DESIGN PROBLEMS IN UNIT II**

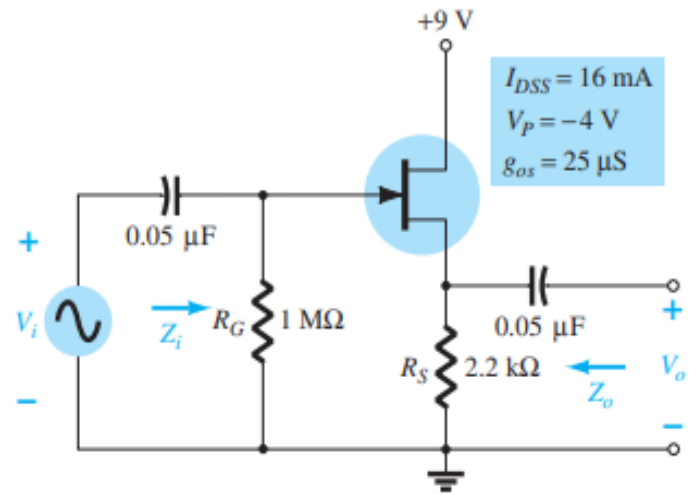**3. EXAMPLE 8.10** A dc analysis of the source-follower network of Fig. 8.32 results in  $V_{GSQ} = -2.86 \text{ V}$  and  $I_{DQ} = 4.56 \text{ mA}$ .

- Determine  $g_m$ .
- Find  $r_d$ .
- Determine  $Z_i$ .
- Calculate  $Z_o$  with and without  $r_d$ . Compare results.
- Determine  $A_v$  with and without  $r_d$ . Compare results.



**Solution:**

a.  $g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(16 \text{ mA})}{4 \text{ V}} = 8 \text{ mS}$

$$g_m = g_{m0} \left( 1 - \frac{V_{GSQ}}{V_P} \right) = 8 \text{ mS} \left( 1 - \frac{(-2.86 \text{ V})}{(-4 \text{ V})} \right) = 2.28 \text{ mS}$$

b.  $r_d = \frac{1}{g_{os}} = \frac{1}{25 \mu\text{S}} = 40 \text{ k}\Omega$

c.  $Z_i = R_G = 1 \text{ M}\Omega$

d. With  $r_d$ ,

$$\begin{aligned} Z_o &= r_d \parallel R_S \parallel 1/g_m = 40 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega \parallel 1/2.28 \text{ mS} \\ &= 40 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega \parallel 438.6 \Omega \\ &= 362.52 \Omega \end{aligned}$$

which shows that  $Z_o$  is often relatively small and determined primarily by  $1/g_m$ .  
Without  $r_d$ ,

$$Z_o = R_S \parallel 1/g_m = 2.2 \text{ k}\Omega \parallel 438.6 \Omega = 365.69 \Omega$$

which shows that  $r_d$  typically has little effect on  $Z_o$ .

e. With  $r_d$ ,

$$\begin{aligned} A_v &= \frac{g_m(r_d \parallel R_S)}{1 + g_m(r_d \parallel R_S)} = \frac{(2.28 \text{ mS})(40 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega)}{1 + (2.28 \text{ mS})(40 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega)} \\ &= \frac{(2.28 \text{ mS})(2.09 \text{ k}\Omega)}{1 + (2.28 \text{ mS})(2.09 \text{ k}\Omega)} = \frac{4.77}{1 + 4.77} = 0.83 \end{aligned}$$

which is less than 1, as predicted above.


Without  $r_d$ ,

$$\begin{aligned} A_v &= \frac{g_m R_S}{1 + g_m R_S} = \frac{(2.28 \text{ mS})(2.2 \text{ k}\Omega)}{1 + (2.28 \text{ mS})(2.2 \text{ k}\Omega)} \\ &= \frac{5.02}{1 + 5.02} = 0.83 \end{aligned}$$

which shows that  $r_d$  usually has little effect on the gain of the configuration.

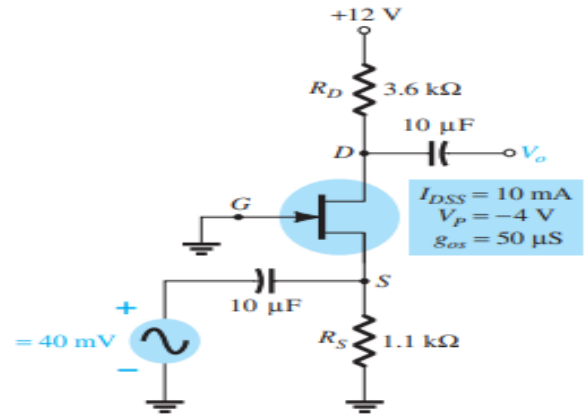3. In the common-gate variety, a close examination will reveal that it has all the characteristics of Figure given below. If  $V_{GSQ} = -2.2 \text{ V}$  and  $I_{DQ} = 2.03 \text{ mA}$ :

- Determine  $g_m$ .
- Find  $r_d$ .
- Calculate  $Z_i$  with and without  $r_d$ . Compare results.
- Find  $Z_o$  with and without  $r_d$ . Compare results.
- Determine  $V_o$  with and without  $r_d$ . Compare results.



**Solution:**

$$\text{a. } g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(10 \text{ mA})}{4 \text{ V}} = 5 \text{ mS}$$

$$g_m = g_{m0} \left( 1 - \frac{V_{GSQ}}{V_P} \right) = 5 \text{ mS} \left( 1 - \frac{(-2.2 \text{ V})}{(-4 \text{ V})} \right) = 2.25 \text{ mS}$$

$$\text{b. } r_d = \frac{1}{g_{os}} = \frac{1}{50 \mu\text{S}} = 20 \text{ k}\Omega$$

c. With  $r_d$ ,

$$\begin{aligned} Z_i &= R_S \parallel \left[ \frac{r_d + R_D}{1 + g_m r_d} \right] = 1.1 \text{ k}\Omega \parallel \left[ \frac{20 \text{ k}\Omega + 3.6 \text{ k}\Omega}{1 + (2.25 \text{ mS})(20 \text{ k}\Omega)} \right] \\ &= 1.1 \text{ k}\Omega \parallel 0.51 \text{ k}\Omega = 0.35 \text{ k}\Omega \end{aligned}$$

Without  $r_d$ ,

$$\begin{aligned} Z_i &= R_S \parallel 1/g_m = 1.1 \text{ k}\Omega \parallel 1/2.25 \text{ ms} = 1.1 \text{ k}\Omega \parallel 0.44 \text{ k}\Omega \\ &= 0.31 \text{ k}\Omega \end{aligned}$$

Even though the condition  $r_d \geq 10R_D$  is not satisfied with  $r_d = 20 \text{ k}\Omega$  and  $10R_D = 36 \text{ k}\Omega$ , both equations result in essentially the same level of impedance. In this case,  $1/g_m$  was the predominant factor.

d. With  $r_d$ ,

$$Z_o = R_D \parallel r_d = 3.6 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 3.05 \text{ k}\Omega$$

Without  $r_d$ ,

$$Z_o = R_D = 3.6 \text{ k}\Omega$$

Again the condition  $r_d \geq 10R_D$  is not satisfied, but both results are reasonably close.  $R_D$  is certainly the predominant factor in this example.

e. With  $r_d$ ,

$$A_v = \frac{\left[ g_m R_D + \frac{R_D}{r_d} \right]}{\left[ 1 + \frac{R_D}{r_d} \right]} = \frac{\left[ (2.25 \text{ mS})(3.6 \text{ k}\Omega) + \frac{3.6 \text{ k}\Omega}{20 \text{ k}\Omega} \right]}{\left[ 1 + \frac{3.6 \text{ k}\Omega}{20 \text{ k}\Omega} \right]}$$

$$= \frac{8.1 + 0.18}{1 + 0.18} = 7.02$$

and  $A_v = \frac{V_o}{V_i} \Rightarrow V_o = A_v V_i = (7.02)(40 \text{ mV}) = 280.8 \text{ mV}$

Without  $r_d$ ,

$$A_v = g_m R_D = (2.25 \text{ mS})(3.6 \text{ k}\Omega) = 8.1$$

with  $V_o = A_v V_i = (8.1)(40 \text{ mV}) = 324 \text{ mV}$

In this case, the difference is a little more noticeable, but not dramatically so.

**5. Design an MOSFET based amplifier using following parameters  $V_{GSQ} = 0.35 \text{ V}$  and  $I_{DQ} = 7.6 \text{ mA}$ .**

**a. Determine  $g_m$  and compare to  $g_{m0}$ .**


**b. Find  $r_d$ .**

**c. Sketch the ac equivalent network for Fig. below.**

**d. Find  $Z_i$ .**

**e. Calculate  $Z_o$ .**

**f. Find  $A_v$ .**

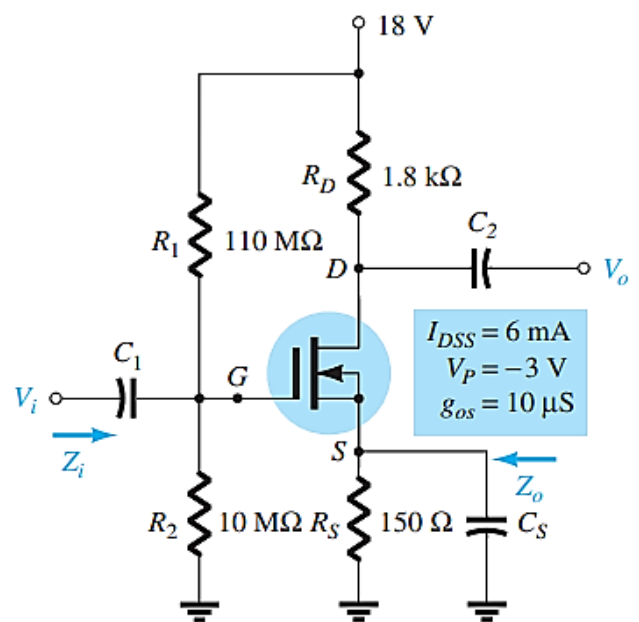


**Solution:**

$$\text{a. } g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(6 \text{ mA})}{3 \text{ V}} = 4 \text{ mS}$$

$$g_m = g_{m0} \left( 1 - \frac{V_{GSQ}}{V_P} \right) = 4 \text{ mS} \left( 1 - \frac{(+0.35 \text{ V})}{(-3 \text{ V})} \right) = 4 \text{ mS} (1 + 0.117) = 4.47 \text{ mS}$$

$$\text{b. } r_d = \frac{1}{y_{os}} = \frac{1}{10 \mu\text{S}} = 100 \text{ k}\Omega$$

c. See Fig. 8.35. Note the similarities with the network of Fig. 8.23. Equations (8.28) through (8.32) are therefore applicable.

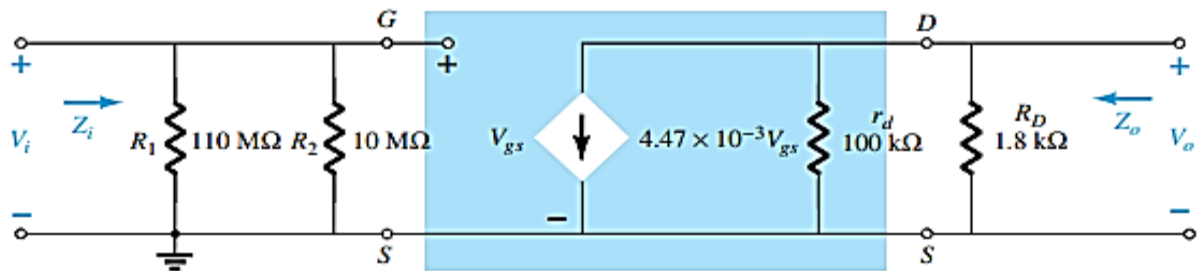

**FIG. 8.35**

AC equivalent circuit for Fig. 8.34.

$$\text{d. Eq. (8.28): } Z_i = R_1 \parallel R_2 = 10 \text{ M}\Omega \parallel 110 \text{ M}\Omega = 9.17 \text{ M}\Omega$$


$$\text{e. Eq. (8.29): } Z_o = r_d \parallel R_D = 100 \text{ k}\Omega \parallel 1.8 \text{ k}\Omega = 1.77 \text{ k}\Omega \approx R_D = 1.8 \text{ k}\Omega$$

$$\text{f. } r_d \geq 10R_D \rightarrow 100 \text{ k}\Omega \geq 18 \text{ k}\Omega$$

$$\text{Eq. (8.32): } A_v = -g_m R_D = -(4.47 \text{ mS})(1.8 \text{ k}\Omega) = 8.05$$
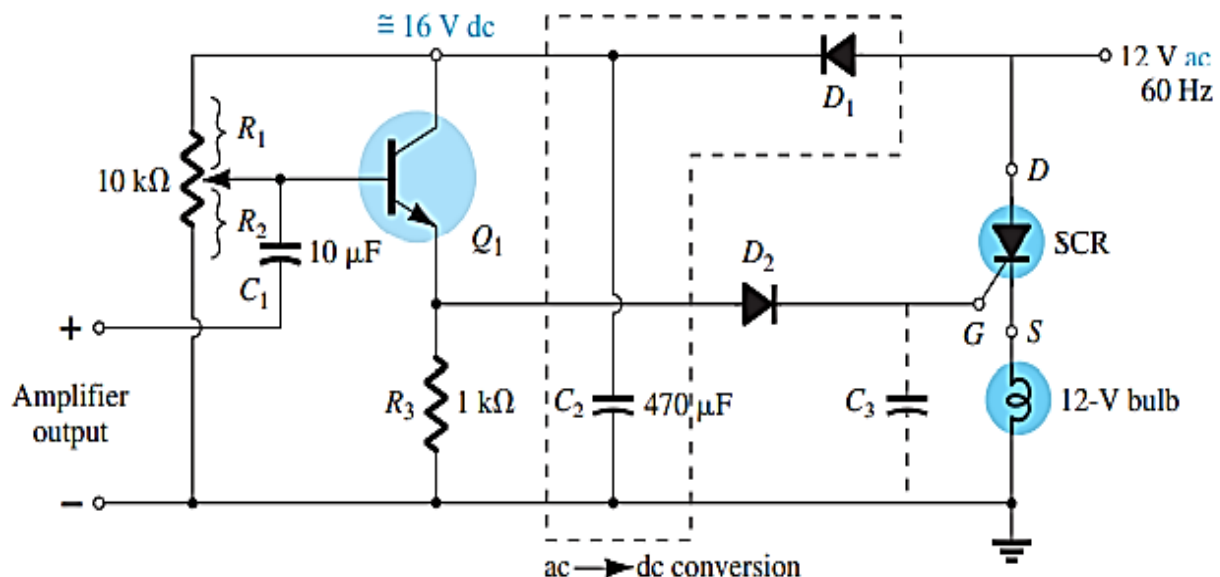
## Design and working of Sound-Modulated Light Source

The light from the 12-V bulb of figure below will vary at a frequency and an intensity that are sensitive to the applied signal. The applied signal may be the output of an acoustical amplifier, a musical instrument, or even a microphone. Of particular interest is the fact that the applied voltage is 12 V ac rather than the typical dc biasing supply.



The immediate question, in the absence of a dc supply, is how the dc biasing levels for the transistor will be established. In actuality, the dc level is obtained through the use of diode D1 , which rectifies the ac signal, and capacitor C2 , which acts as a power supply filter to generate a dc level across the output branch of the transistor. The peak value of a 12-V rms supply is about 17 V, resulting in a dc level after the capacitive filtering in the neighbourhood of 16 V. If the potentiometer is set so that R1 is about 320, the voltage from base to emitter of the transistor will be about 0.5 V, and the transistor will be in the “off” state. In this state the collector and emitter currents are essentially 0 mA, and the voltage across resistor R3 is approximately 0 V. The voltage at the junction of the collector terminal and the diode is therefore 0 V, resulting in D2 being in the “off” state and 0 V at the gate terminal of the silicon-controlled rectifier (SCR).